

# Boolean Logic

Digital Systems 2022/23

Dr James Stovold

# Boolean Algebra

(George Boole, 1815–64)

- Foundation of logical operations within computers.
- Variables are either True (T) or False (F).
  - Mutually-exclusive characters map nicely to binary numbers!
- Fundamental operations are conjunction (and), disjunction (or), negation (not).

# Conjunction

(AND)

- Conjunction is represented by  $\wedge$  · or <nothing> (& or && in C)
  - Similar to product in elementary algebra

$$Q = AB = A \cdot B$$

$$Q = A \wedge B$$

Truth  
table



A	B	Q
F	F	F
F	T	F
T	F	F
T	T	T

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1



Also a  
truth  
table

# Disjunction

(OR)

- Disjunction is represented by  $\vee$  or  $+$  ( $|$  or  $||$  in C)
  - Similar to addition in elementary algebra

$$Q = A + B$$

$$Q = A \vee B$$

A	B	Q
F	F	F
F	T	T
T	F	T
T	T	T

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

# Negation

## (NOT)

- Negation is represented by  $\neg$  or ' ( $\sim$  or ! in C)
  - $\bar{X}$  is pronounced "X bar",  $X'$  is "X prime"

$$Q = \neg A$$

$$Q = A' = \bar{A}$$

A	Q
F	T
T	F

A	Q
0	1
1	0

# Negated Operators

## (NAND, NOR)

- Represented by a combination:
  - NAND (NOT AND), e.g. NOT(X AND Y),  $\overline{XY}$
  - NOR (NOT OR), e.g. NOT(X OR Y),  $\overline{X + Y}$

$$Q = \neg(A \wedge B)$$

A	B	AB	Q
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

$$Q = \neg(A \vee B)$$

A	B	A + B	Q
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

# Exclusive-OR/-NOR

(XOR, XNOR)

- Exclusive-OR is represented by  $\oplus$  ( $\wedge$  in C)
- Exclusive-NOR is represented by  $\odot$

$$Q = A \oplus B$$

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

$$Q = A \odot B$$

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

# Quick aside: Truth Tables

- The truth table is a useful technique for mapping out an entire function.
- We list all possible permutations of the input variables and calculate the output variables.
- Particularly useful for working through a complicated equation.



# Truth Table Examples

$$Q = AB + C$$

A	B	C	AB	Q
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

# Truth Table Examples

$$Q = AB + C$$

A	B	C	AB	Q
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

# Truth Table Examples

$$Q = AB + C$$

A	B	C	AB	Q
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	0	
1	0	1	0	
1	1	0	1	
1	1	1	1	

# Truth Table Examples

$$Q = AB + C$$

A	B	C	AB	Q
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	0	
1	0	1	0	
1	1	0	1	
1	1	1	1	



# Truth Table Examples

$$Q = AB + C$$



A	B	C	AB	Q
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	1
1	1	1	1	1
  
# Logic Gates

- Each of our operators has a conceptual electronic component/symbol:





Negation  
"Bubble"

 
 

  
# Logic Gates

- Each of our operators has a conceptual electronic component/symbol:



Negation  
"Bubble"

 
 


# Universal Gates



- NAND and NOR gates are considered "universal" gates
- Any binary logic can be built just from NAND gates, or just from NOR gates.
  - Remember: simple is cheap, simple is good!




# Using NANDs

  


# Using NANDs

  

# Using NANDs

 

A	B
0	0
0	1
1	0
1	1

 

# Boolean Algebra

Law	AND form	OR form
Identity 1	$A = \overline{\overline{A}}$	$A = \overline{\overline{A}}$
Identity 2	$1A = A$	$0 + A = A$
Null	$0A = 0$	$1 + A = 1$
Idempotence	$AA = A$	$A + A = A$
Complementarity	$A\overline{A} = 0$	$A + \overline{A} = 1$
Commutativity	$AB = BA$	$A + B = B + A$
Associativity	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributivity	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption	$A(A + B) = A$	$A + AB = A$
de Morgan's Law	$\overline{AB} = \overline{A} + \overline{B}$	$\overline{A + B} = \overline{A} \cdot \overline{B}$

# Proof by Perfect Induction

(AND Forms)

$A = \overline{\overline{A}}$		
$A$	$\overline{A}$	$\overline{\overline{A}}$
0	1	0
1	0	1

$1A = A$		
1	$A$	$1A$
1	0	0
1	1	1

$0A = 0$		
0	$A$	$0A$
0	0	0
0	1	0

$AA = A$		
$A$	$A$	$AA$
0	0	0
1	1	1

$A\overline{A} = 0$		
$A$	$\overline{A}$	$A\overline{A}$
0	1	0
1	0	0

$A(A + B) = A$			
$A$	$B$	$A + B$	$A(A + B)$
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

# de Morgan's Law

- $\overline{(AB)} = \bar{A} + \bar{B}$  and  $\overline{(A + B)} = \bar{A} \cdot \bar{B}$
- Useful for restating expressions
- If all sub-expressions are ANDed together, we can switch to ORing them together:
  1. negate overall expression
  2. negate all sub-expressions
  3. switch between ANDs and ORs

# Designing Logic Circuits

- Basic approach:
  1. Write out a truth table for the desired logical function
  2. Derive a Boolean expression by ORing together all the rows whose output column is 1
  3. Translate to logic gates
    - Can simplify using digital circuit analysis techniques (see later lecture).

# Logic Circuit Design

## Example

- Consider a lighting system for a house.
- You have a light over the stairs which is controlled by two switches:
  - one at the bottom, in the hallway (H)
  - one at the top of the stairs (S)
- We want to be able to switch the light on at the bottom and off again at the top (and vice-versa).



# Stairway Light Logic

- We want the light to be **on** if S is **up** and H is **down**.
- Alternatively, the light should be **on** if S is **down** and H is **up**.

	S	H	Light
$\bar{S}H$	0	0	0
	0	1	1
$S\bar{H}$	1	0	1
	1	1	0

# Stairway Light Logic

- So,  $L = \bar{S}H + S\bar{H}$  (in sum-of-products form)
- We can implement this using NAND gates.
- Apply de Morgan's law:
  - Let  $X = \bar{S}H$  and  $Y = S\bar{H}$ , so we have  $X + Y$
  - By de Morgan's:  $X + Y = \overline{(\bar{X}\bar{Y})}$
  - Expand:  $L = \overline{(\overline{(\bar{S}H)} \overline{(S\bar{H})})}$
  - This is now in the required 'Inverted AND' form...

